

M.Sc. 1st Semester Examination, 2013

ELECTRONICS

(Analog Electronics)

[Theory]

PAPER —ELC-104

Full Marks : 50

Time : 2 hours

Answer Q. No. 1 and any three from the rest

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words.as far as practicable

Illustrate the answers wherever necessary

1. Answer all questions : 2 × 5

- (a) With the help of frequency response curve at a first order high pass filter explain its roll off rate.**

(Turn Over)

- (b) What is the advantage of SMPS over linear voltage regulator ?
 - (c) Why synchronizing pulses are used in television system ?
 - (d) Why harmonics would be produced in an amplifier ?
 - (e) Draw the equivalent electrical circuit of a piezoelectric crystal.
2. (a) Explain Schmitt trigger with suitable circuit diagram. Give input and output waveforms. 5
- (b) Draw the circuit diagram of an active high pass second order Butterworth filter and explain its operation. Derive the expression of the transfer function. 5
3. (a) Give the block diagram of a standard power supply unit. 2
- (b) Explain the principle of operation of a series voltage regulator using op-amp. 3

- (c) Explain a BUCK converter using suitable circuit diagram. 5
4. (a) Mention, two natural substances which shows piezoelectric effect. 2
- (b) Draw Pierce crystal oscillator and mention the working of each of the component. 3
- (c) Give the circuit diagram and describe the operation of a triangular wave generator. Derive the expression for frequency at output signal. 5
5. (a) Explain working principle of PLL. What are capture-in-range and lock-in-range ? 5
- (b) Describe how picture transmission takes place in case of monochrome television. 5
6. (a) Write down the advantages of class-C amplifier over other amplifiers. 2
- (b) A class-C transistor amplifier is operating at 150 kHz. The transistor is conducting for

(4)

1 μ s in each cycle. The saturation values for the transistor are $I_{C(SAT)} = 100$ mA

$$V_{CE(Sat)} = 0.2 \text{ V}$$

Assuming ideal pulse approximation and the output swinging over the entire load line, find the average power dissipation. 3

- (c) What do you mean by transducer and sensor? Explain the action of a photo transducer with a suitable diagram. 2 + 3

[*Internal Assessment* : 10 Marks]
