

2014

M.Sc.

4th Semester Examination

ELECTRONICS

PAPER—ELC-405

(PRACTICAL)

Full Marks 150

Time : 3 hours

The figures in the right-hand margin indicate full marks.

(Advanced Electronics Lab)

Answer any one question selecting it by a lucky draw.

In each of the following questions, you have to save the design file by "your roll no., — design" and then save the plot in a file "your roll no., — slot".

1. Design an inverting amplifier circuit using OP-AMP taking input resistor $R_1 = 1 \text{ K}\Omega$, feedback resistor $R_2 = 6.8 \text{ K}\Omega$ and load resistor $R_3 = 10 \text{ K}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Stimulate the circuit using PSPICE and plot the input voltage (V_{in}) vs. time and output voltage (V_0) vs. time in the same graph. Also verify the gain of the amplifier with the given value.

(Turn Over)

2. Design a first order high pass active filter with cut-off frequency 1 KHz in PSPICE. Stimulate the circuit and plot the gain *vs.* frequency curve. Also verify the cut-off frequency of the plot with its given value.
3. Design a non-inverting amplifier circuit using OP-AMP taking input resistor $R_1 = 1\text{K}\Omega$, feedback resistor $R_2 = 8.2\text{ K}\Omega$ and load resistor $R_3 = 10\text{ K}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage V_{in} *vs.* time and output voltage V_0 *vs.* time in same graph. Also verify the gain of the amplifier with given value.
4. Design a second order active low pass Butterworth filter with cut-off frequency 3 KHz. Simulate the circuit PSPICE and slot the gain *vs.* frequency curve. Also verify the cut-off frequency with the given value.
5. Design a astable multivibrator circuit with frequency 1 KHz and duty cycle 66.67% using IC 555. Simulate the circuit using PSPICE and plot the output voltage *vs.* time curve. Also verify the output frequency and duty cycle of the plot with their given values.
6. Design a first order low pass active filter with cut-off frequency 3 KHZ in PSPICE. Simulate the circuit and plot the gain *vs.* frequency curve. Also verify the cut-off frequency from the plot with its given value.

7. Design a second order active high pass Butterworth filter with cut-off frequency 1 KHz. Simulate the circuit using PSPICE and plot the gain *vs.* frequency curve. Also verify the cut-off frequency with the given value.
8. Design a non-inverting amplifier circuit using OP-AMP taking input resistor $R_1 = 1 \text{ K}\Omega$, feedback resistor $R_2 = 10 \text{ K}\Omega$ and load resistor $R_3 = 10 \text{ K}\Omega$. Apply sine wave as an input signed with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage (V_{in}) *vs.* time and output voltage (V_o) *vs.* time in same graph. Also verify the gain of the amplifier with gain value.
9. Construct AND, OR and NOT gates using MOSFETs. Also verify their truth tables.
10. Design a 3 bit synchronous even counter using J-K flop-flop. Verify the count sequence by LED display.
11. Design a 3 bit synchronous odd counter using J-K flop-flop. Verify the count sequence by LED display.
12. Design a MOD-5 synchronous up counter using J-K flip-flop. Verify the count sequence by LED display.

Marks Distribution (for PSPICE)

For Question Nos. 1 to 8 :

	<i>Marks</i>
Theory	: 07
Circuit Design	: 10
Simulation	: 10
Verification & Accuracy	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
Total	: 50 Marks

Marks distribution (for digital)

For Question Nos. 9 to 12 :

	<i>Marks</i>
Theory	: 05
Circuit Design	: 15
Implementation	: 07
Experimental Result	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
Total	: 50 Marks