

2014

M.Sc.

1st Semester Examination

ELECTRONICS

PAPER—ELC-103

Full Marks : 50

Time : 2 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.


Illustrate the answers wherever necessary.

(Network Analysis and Synthesis)

Answer Q. No. 1 and any three questions from the rest.

1. Answer all questions : 2×5

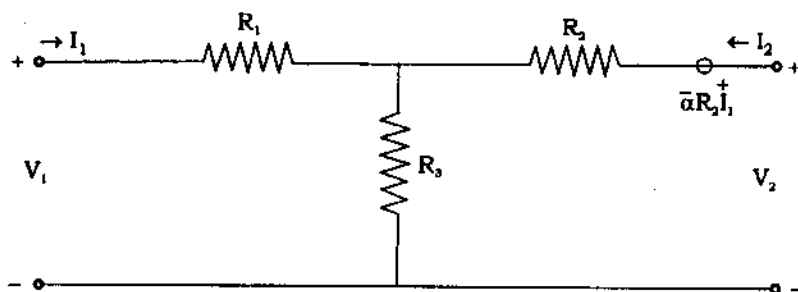(a) Find the impedance matrix $[Z]$ of the following circuit : 2×5




(Turn Over)

- (b) What information you may get from the pole-zero plot ?
- (c) If Z_{11} of a network is as follows, then draw the network :


$$Z_{11} = S + \frac{1}{S + \frac{1}{S}}$$

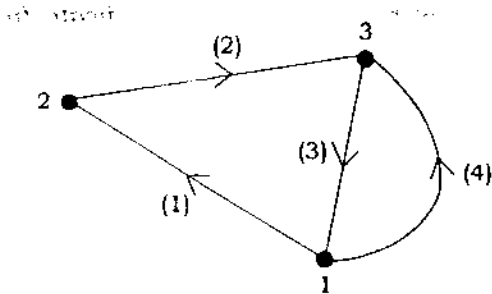- (d) Determine the number of possible trees of the following network :



- (e) Explain the even function symmetry, odd function symmetry and half wave symmetry in connection with Fourier series.

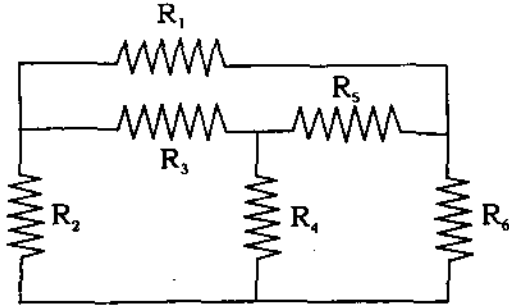2. (a) Draw a network graph for the network shown below :




- (b) The reduced incidence matrix of an oriented graph is :

$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$


Draw the graph.

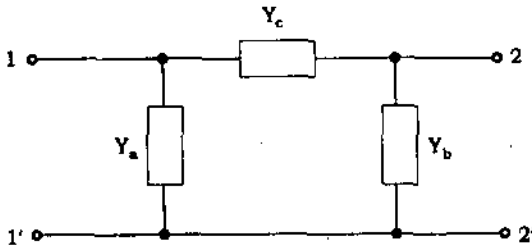- (c) Find out the admittance matrix of the following circuit :



3+4+3

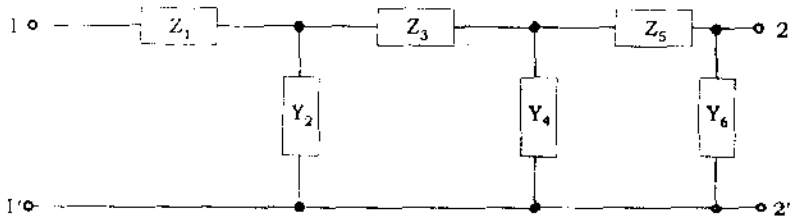3. (a) A general ladder network is shown below : State the driving point impedance at port 1 with port 2 open :




- (b) Let us consider the following function :

$$H(S) = 20 \left(1 + \frac{s}{100} \right); \text{ Symbols have their usual meanings.}$$

Sketch its Bode plot.

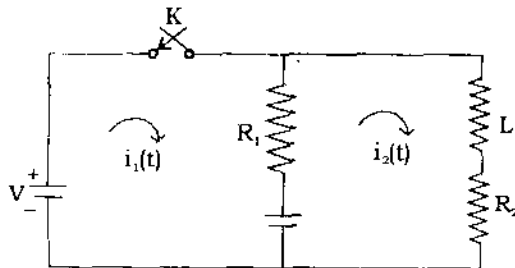- (c) A network is shown below. Find the expression for $i_1(s)$ and $i_2(s)$ when the switch is closed :




- (d) A function in Laplace domain is given by :

$$F(s) = \frac{2}{s} - \frac{1}{s+3}$$


Obtain its value by final value theorem in t domain.

2+4+2+2

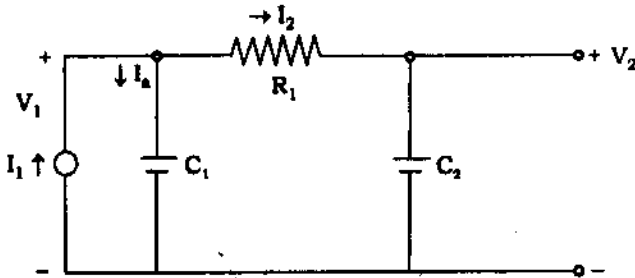4. (a) Find out the current gain $\alpha_{12}(s)$ and transfer impedance $Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$, $\alpha_{12}(s) = \frac{I_2(s)}{I_1(s)}$ of the following circuit :




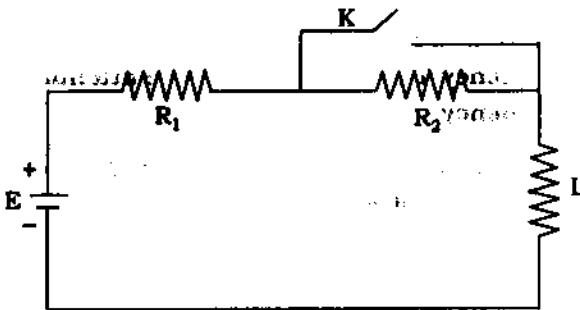- (b) In the given figure, the battery voltage is applied for a steady state period. Obtain the compute expression for the current after closing the switch K. Assume $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1H$, and $E = 10V$.



5+5

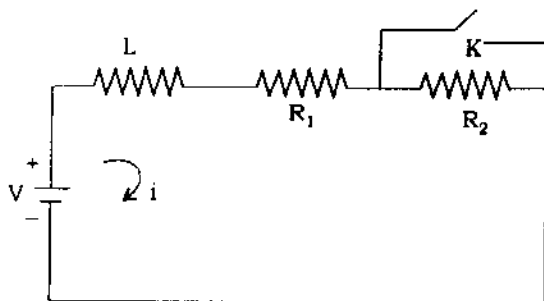5. (a) Show that the nominal characteristics impedance of a constant K filter is $\sqrt{\frac{L}{C}}$.
- (b) For the network shown below the switch K is closed at $t = 0$. Determine the current i in the circuit :



5+5

6. (a) Design a constant - K low-pass T section filter with a nominal resistance of 50Ω to produce cut off at a frequency 1.2 KHz. Find out the attenuation at 2 KHz frequency.
- (b) Determine the expression for the driving point impedance of a relative network which has poles at $\omega = 0, 4000$ rad/s and α , zeros are to be located at $\omega = 2000$ and 6000 rad/s. The impedance is to be $-j 700$ ohm at 1000 rad/s. 5+5

[Internal Assessment — 10 Marks]
