

2014

M.Sc.

1st Semester Examination

ELECTRONICS

PAPER—ELC-106

(PRACTICAL)

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

(Electronic Circuit Lab)

Answer any one question, selecting it by a lucky draw.

1. Design a regulated power supply using a 78XX series of IC regulator and study its performance :

Output Voltage : V

Output Current : mA

- | | |
|--|-----|
| (a) Working formula | 4 |
| (b) Draw of circuit diagram with labelling | 3 |
| (c) Circuit implementation on breadboard | 3 |
| (d) Recording of data for getting the characteristics of load and line regulations | 5+5 |

(Turn Over)

- (e) Drawing of graphs 4+4
- (f) Calculation of percentage regulation and stability factor 2+2
- (g) Discuss the results obtained 3
2. Design a small stage active low pass Butter-worth filter and study its performance :
- Cut of Frequency : kHz
- Gain :
- (a) Working formula 4
- (b) Circuit diagram with labelling 3
- (c) Design consideration for cut-off frequency
= kHz
- (d) Implementation of the circuit on the bread board 3
- (e) Recording of data for frequency response characteristics 8
- (f) Drawing of graph 5
- (g) Finding and compression of the cut-off frequency and roll-off rate with the known value 3+2+3+2
- (h) Discussion of the result obtained 2
3. Design a regulated power supply of variable output using LM 317 :
- Output Voltage : 6V to 10V
- Output Current : 250 mA
- (a) Working formula 4
- (b) Circuit diagram with labelling 3
- (c) Circuit Implementation on bread board 3

- (d) Recording of data for load and line regulations 5+5
- (f) Drawing of graphs 4+4
- (g) Calculation of percentage of regulation and stability factor 2+2
- (h) Discussuion of the results obtained 3
4. Study the performance of an antilogarithmic amplifier using OPAMP :
- (a) Working Principle 4
- (b) Drawing of circuit diagram with labelling 3
- (c) Circuit Implementation on bread board 3
- (d) Recording of data by varying the input voltage at small steps 10
- (e) Drawing of graphs 4+4
- (f) Discussuion of the results obtained 3
- (g) Comment on possible application on the circuit 4
5. Design of R-C coupled amplifier using transistors and study its performance :
- (a) Working formula 4
- (b) Circuit diagram with labelling 3
- (c) Design consideration for gain ... 5
- (d) Recording of data for frequency response characteristics 10
- (e) Drawing of graphs 4
- (f) Calculation of bandwidth 3
- (g) Implementation of the circuit of bread board 3
- (h) Discussion of the results obtained 3

6. Design a regulated power supply using power transistor as pass element and an OP-AMP as comparator :

Output Voltage : V

Output Current : mA

- | | |
|--|-----|
| (a) Working formula | 4 |
| (b) Circuit diagram with labelling | 3 |
| (c) Design considerations | 4 |
| (d) Circuit implementation on bread board | 4 |
| (e) Recording of data for load and line regulations | 4+4 |
| (f) Drawing of graphs | 3+3 |
| (g) Calculation of percentage of regulation and stability factor | 2+2 |
| (h) Discussions of the results obtained | 2 |
7. Design a second order active high pass Butter-worth filter and study its performance :
- | | |
|--|-------------|
| (a) Working formula | 4 |
| (b) Circuit diagram with labelling | 3 |
| (c) Design consideration for cut-off frequency = ... kHz and gain = ... | 5 |
| (d) Implementation of the circuit on bread board | 3 |
| (e) Recording of data for frequency response characteristics | 8 |
| (f) Drawing of graphs | 4 |
| (g) Finding and compression of the cut-off frequency and roll-off rate with known values | (2+1)+(2+1) |
| (h) Discussions of the results obtained | 2 |

8. Design an active high pass Butter-worth filter with cut-off frequency = ... kHz and pass band gain = ... using one R-C section and study its performance :
- | | |
|--|-------------------------------------|
| (a) Working formula | 4 |
| (b) Circuit diagram with labelling | 3 |
| (c) Design consideration | 4 |
| (d) Implementation of the circuit | 3 |
| (e) Recording of data for frequency response characteristics | 8 |
| (f) Drawing of graphs | 4 |
| (g) Finding and compression of the cut-off frequency and roll-off rate with known values | $(2+1\frac{1}{2})+(2+1\frac{1}{2})$ |
| (h) Discussions of the results obtained | 2 |
9. Study the performance of a logarithmic amplifier using OP-AMP :
- | | |
|---|-----|
| (a) Working formula | 4 |
| (b) Circuit diagram with labelling | 3 |
| (c) Design considerations and components to be used | 3 |
| (d) Recording of data | 10 |
| (e) Drawing of graphs | 4+4 |
| (f) Discuss the nature of the graph obtained and also the results | 3 |
| (h) Comment on possible application of the circuit using the results obtained | 4 |

10. Design an active low pass Butterworth filter with a roll-off rate 20 dB/decade having cut off frequency ...kHz and pass band gain of 2. Study its performance :
- | | |
|---|-------------------------------------|
| (a) Working formula | 4 |
| (b) Circuit diagram with labelling | 3 |
| (c) Design considerations | 2 |
| (d) Implementation of the circuit on bread board | 3 |
| (e) Recording of data for frequency response characteristics | 8 |
| (f) Drawing of graphs | 3 |
| (g) Finding and comparison of cut-off frequency and roll-off rate with supplied value | $(2+1\frac{1}{2})+(2+1\frac{1}{2})$ |
| (h) Discussion of the results obtained | 2 |

Distribution of Marks

| | |
|----------------------|------------|
| Experiment | : 35 Marks |
| Viva-Voce | : 10 Marks |
| Laboratory Note Book | : 05 Marks |
| Total | : 50 Marks |