

**Marks Distribution (for PSPICE)**

For Question Nos. 1 to 10 :

	<i>Marks</i>
Theory	: 07
Circuit Design	: 10
Simulation	: 10
Verification & Accuracy	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
<hr/>	
<b>Total</b>	<b>: 50 Marks</b>

Marks distribution (for digital)

For Question Nos. 11 & 12 :

	<i>Marks</i>
Theory	: 05
Circuit Design	: 15
Implementation	: 07
Experimental Result	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
<hr/>	
<b>Total</b>	<b>: 50 Marks</b>

7. Design a second order active low pass Butterworth filter with cut-off frequency 5 KHz. Simulate the circuit using PSPICE and plot the gain *vs.* frequency curve. Also verify the cut-off frequency with the given value.
8. Design a astable multivibrator circuit with frequency 2 KHz and duty cycle 75% using IC – 555. Simulate the circuit using PSPICE and plot the output voltage *vs.* time curve. Also verify the output frequency and duty cycle of the plot with their given values.
9. Design an integrator circuit using OP-AMP taking input resistor  $R_1 = 1 \text{ K}\Omega$  feedback resistor  $R_2 = 6.8 \text{ K}\Omega$ , feedback capacitor  $C_2 = 0.1 \text{ }\mu\text{F}$  and load resistor  $R_3 = 16 \text{ K}\Omega$ . Stimulate the circuit using PSPICE and plot the transient response of the output voltage for a suitable input voltage.
10. Design a differentiator circuit using OP-AMP taking input resistor  $R_1 = 1 \text{ K}\Omega$  , input capacitor  $C_1 = 0.4 \text{ }\mu\text{F}$ , feedback resistor  $R_2 = 6.8 \text{ K}\Omega$ . and load resistor  $R_3 = 10 \text{ K}\Omega$ . Stimulate the circuit using PSPICE and plot the transient response of the output voltage for a suitable input voltage.
11. Construct AND or and NOT gates using MOSFETs. Also verify their truth tables.
12. Design a 3-bit synchronous even counter using J-K flip-flop. Verify the count sequence by LED display.

- sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage  $V_{in}$  vs. time and output voltage  $V_0$  vs. time in same graph. Also verify the gain of the amplifier with given value.
3. Design a second order active high pass Butterworth filter with cut-off frequency 3 KHz. Simulate the circuit using PSPICE and plot the gain vs. frequency curve. Also verify the cut-off frequency with the given value.
  4. Design a astable multivibrator circuit with frequency 3 KHz and duty cycle 66-67% using IC 555. Simulate the circuit using PSPICE and plot the output voltage vs. time curve. Also verify the output frequency and duty cycle of the plot with their given values.
  5. Design a first order low pass active filter with cut-off frequency 1 KHz in PSPICE. Simulate the circuit and plot the gain vs. frequency curve. Also verify the cut-off frequency from the plot with its given value.
  6. Design an inverting amplifier circuit using OP-AMP taking input resistor  $R_1 = 1 \text{ K}\Omega$ , feedback resistor  $R_2 = 10 \text{ K}\Omega$  and load resistor  $R_3 = 10 \text{ K}\Omega$ . Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage ( $V_{in}$ ) vs. time and output voltage ( $V_0$ ) vs. time in same graph. Also verify the gain of the amplifier with given value.

**2015**

**M.Sc.**

**4th Semester Examination**

**ELECTRONICS**

**PAPER—ELC-405**

**(PRACTICAL)**

*Full Marks : 50*

*Time : 3 hours*

*The figures in the right-hand margin indicate full marks.*

**(Advanced Electronics Lab)**

Answer any *one* question selecting it by a lucky draw.

*In each of the following questions, you have to save the design file by "your roll no., — design" and then save the plot in a file "your roll no., — plot".*

1. Design a first order high pass active filter with cut off frequency 5 KHz in PSPICE. Stimulate the circuit and plot the gain Vs. frequency curve. Also verify the cut off frequency of the plot with given value.
2. Design a non-inverting amplifier circuit using OP-AMP taking input resistor  $R_1 = 1\text{K}\Omega$ , feedback resistor  $R_2 = 8.2\text{K}\Omega$  and load resistor  $R_3 = 10\text{K}\Omega$ . Apply

*(Turn Over)*