

2019

**DIGITAL ELECTRONICS**

PAPER – 1104

*Full Marks : 100*

*Time : 3 hours*

Answer **Q.No. 1** and any **four** from the rest

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

1. Answer any *five* questions : 2 × 5
- (a) State De Morgan's theorem.
  - (b) What is combinational circuit? Give example.
  - (c) Define min term and max term.

( Turn Over )

- (d) Define latch.
- (e) Compare EEPROM and flash memory.
- (f) Define shift register.
- (g) Convert B64.53 to binary.
- (h) Define the term propagation delay and hold time.

2. (a) Simplify the following expression using k-map method

$$F(w, x, y, z) = \sum_m (7, 9, 10, 11, 12) + \sum_d (2, 4)$$

- (b) Implement a full adder using NAND gates only and explain the working procedures using truth table.

8 + 7

3. (a) What is decoder? Design a 3 to 8 line decoder and explain its operation with a truth table.

- (b) What is the difference between Fan-in and Fan-out?

- (c) Design a 8 : 1 MUX using two 4 : 1 MUX and any gates (if required). 8 + 3 + 4

4. (a) What is digital comparator circuit ?  
 (b) Design a 2 bit comparator circuit and explain its operation.  
 (c) Implement the expression using a multiplexer

$$f(A, B, C, D) = \sum_m(0, 2, 3, 6, 8, 9, 12, 14)$$

$2 + 8 + 5$

5. (a) Explain full adder with truth table and logic circuit.  
 (b) Subtract  $(29)_{10} - (7)_{10}$  using 2's complement method.  
 (c) What is BCD addition connection ? Perform BCD addition of 1001 and 0111. 5 + 5 + 5
6. (a) What is flip-flop ?  
 (b) What do you mean by race condition in a flip-flop ?

(c) Design a JK master slave flip-flop and explain its operation.

(d) Express the function  $Y = A + \overline{BC}$  in a canonical SOP form. 2 + 2 + 8 + 3

7. Write short notes on any *three* of the following :

5 × 3

(i) Shift register

(ii) MOD-10 counter

(iii) Seven segment display

(iv) Edge triggering in a flip-flop

(v) BCD addition.

[ *Internal Assessment* : 30 Marks ]

