

2019

B. Sc.

1st Semester Examination

ELECTRONICS (Honours)

Paper : C 1-P

(Practical)

(Basic Ccercular Theory and Network Analysics)

Full Marks : 20

Time : 3 Hours

*The figures in the margin indicate full Marks.
Candidates are required to give their answers in their
own words as far as practiable.*

Answer any one question by selecting it by a lucky draw.

1. Verify Norton's theorm by using resistive Wheatstone Bridge network.
2. Verify Thecenin's theom by using resistive Wheatstone Bridge network.
3. Verify maximum power transfer theorem using resistive Wheatstone Bridge network.

[Turn Over]

4. Design a passive first order low pass filter of cut off frequency $f_c = \dots$ Hz. (Cut-off frequency to be supplied during examination) Study its frequency response.
5. Design a passive high pass filter of cut-off frequency $f_c = \dots$ and study its frequency response (The cut-off frequency to be supplied during examination)
6. Design an integrator circuit using OP-AMP and verify that the circuit is capable of integrating functions.
7. Design a differentiator circuit using OP-AMP and verify that the circuit is capable of differentiating functions.

Distribution of Marks

Experiment : 15 (Th + Ckt -03, data recording 08 plotting or calculation = 04)

Laboratory Note Book. : 02

Viva-Voce. : 03

Total : 20 Marks.
