

2019

3rd Semester Examination
ELECTRONICS (Honours)

Paper - C6P

(Electronic Circuit Lab)

Full Marks : 20

Time : 3 Hours

*The figures in the margin indicate full marks.
Candidates are required to give their answers
in their own words as far as practicable.*

Answer any one questions selecting it by a lucky draw.

1. Design a full wave bridge rectifier circuit and study its input /output waveform.
2. Design a regulated power supply using zener diode and capacitive filter and study its performance.
3. Design a 5V DC regulated power supply and measure its load regulation.
4. Design a clamper circuit and study its input and output characteristics for a sinusoidal wave.

[Turn Over]

5. Design a voltage divider bias and fixed its Q-point.
6. Design class C power amplifier and study its performance.
7. Design a Hartley's oscillator and find its output frequency.
8. Design a colpitt's oscillator and find its oscillating frequency.
9. Design a RC phase shift oscillator circuit and find its output frequency.
10. Design a common source FBT amplifier and study its frequency response characteristics.

Distribution of Marks:

Experiment : 15 Marks

(Th/Ckt = 3, data recording = 8,

plotting of graph and calculations = 4)

Laboratory Note Book : 02 Marks

Viva-voce : 03 Marks

Total : 20 Marks
