

Total Pages - 6

UG/1st Sem/ELEC(H)/Pr/2019

2019

B. Sc.

1st Semester Examination

ELECTRONICS (Honours)

Paper : GE 1-P

(Practical)

Electronics Circuit and PCB Designing Lab

Full Marks : 20

Time : 3 Hours

Candidates are required to give their answers in their own words as far as practicable.

The figures in the margin indicate full marks.

Answer *one* question selecting it by a lucky draw.

(Electronic Circuits and PCB Designing Lab)

Answer *any one* question selectin by a Lucky draw.

1. Verify Thevenin's theorem by using a resistive Wheatstone bridge network.

(a) Theory and working formula

3

[Turn Over]

- | | |
|--|----|
| (b) Circuit diagram | 1½ |
| (c) Circuit implementation | 1½ |
| (d) Data for load voltage (V_L) and Load current. | 5 |
| (e) Determination of V_{Th} and R_{Th} from $I_L - V_L$ graph | 3 |
| (f) Accuracy | 1 |
| 2. Verify Superposition theorem (Taking at least two voltage sources) | |
| (a) Theory | 2 |
| (b) Circuit diagram | 2 |
| (c) Circuit implementation | 2 |
| (d) Data for verification | 7 |
| (e) Accuracy | 1 |
| (f) Discussion | 1 |
| 3. Verify Maximum Power transfer theorem by using resistive Wheatstone bridge network. | |
| (a) Theory and working formula | 2 |
| (b) Circuit diagram | 1½ |

- | | |
|---|----|
| (c) Circuit impementation | 1½ |
| (d) Data for load voltage (V_L) and Load current (I_L). | 5 |
| (e) Verification of Maximum power transfer theorem from $R_L - P$ curve | 4 |
| (f) Accuracy | 1 |
4. Study the regulation characteristics of a Half Wave rectifier without any filter and with a shunt capacitor filter for a given input. Determine the ripple factor (ν) and percentage regulation in each case.
- | | |
|--|-------|
| (a) Working formula and schematic circuit diagram. | 2 |
| (b) Circuit implementation | 1 |
| (c) Data for voltage regulation and wave form to be studied in CRO and measurement of ripple factor. | 6+1+1 |
| (d) Voltage regulation curves. | 3 |
| (e) Percentage voltage regulation for a specified current. | |

[Turn Over]

5. Study the regulation characteristics of a centre tapped full wave rectifier without any filter and with a shunt capacitor filter for a given input. Determine the ripple factor (ν) and percentage regulation in each case.

(a) Working formula and schematic circuit diagram.

2

(b) Circuit implementation

1

(c) Data for voltage regulation and wave form to be studied in CRO and measurement of ripple factor.

6+1+1

(d) Voltage regulation curves

3

(e) Percentage voltage regulation for a specified current.

1

6. Study the load regulation characteristics of the Zener diode.

(a) Theory and circuit diagram and circuit implementation.

2+1

(b) Calculation of limiting resistance R_S

1

(c) Data for regulation curve $V_S = 1.6V_Z$, where V_S is the supply voltage and V_Z is the Zener breakdown voltage.

6

- (d) Drawing of load regulation curve 3
- (e) Percentage regulation at specified load current 1
- (f) Accuracy and disension 1
7. Draw the static output characteristics of a transistor in common emitter configuration for three different base currents and to determine r_i , r_o and β_{ac} in the given region.
- (a) Theory and circuit diagram and circuit implementation.
2 + 1
- (b) Circuit diagram and implementation. 2
- (c) Data for output characteristics curves 6
- (d) Drawing of curves and calculation of r_i , r_o and β_{ac} 5
8. Design a CE amplifier with a given transistor [h_{FE} and $(I_B)_{max}$ are to be supplied] for a particular mid-band voltage gain (say $A_V = 50$) and record the data for frequency response for a fixed input voltage and hence find the band with of the amplifier.

(Calculations for the component are to be done)

[Turn Over]

- | | |
|---|---|
| (a) Theory and circuit diagram. | 3 |
| (b) Calculations for the components. | 2 |
| (c) Implementation of the circuit. | 3 |
| (d) Data for frequency response curve | 5 |
| (e) Drawing of frequency response curve | 2 |

Distribution of Marks

Experiment	: 15 marks
L.N.B	: 02 marks
Viva-voce	: 03 marks
<hr/>	
Total	: 20 marks
<hr/>	
