

Total Page - 3

UG/4th Sem/ELEC./H/19

2019

B.Sc. (Hons)

4th Semester Examination

**ELECTRONICS**

Paper - C9T

(Digital Electronics and Verilog/VHDL)

Full Marks : 40

Time : 2 Hours

*The figures in the margin indicate full marks.  
Candidates are required to give their answers  
in their own words as far as practicable.*

1. Answer any five questions : 2×5=10

(i) Convert the following Hexadecimal number to Octal number

$(641A)_{16}$

(ii) Simplify the following :

$AB + \overline{AC} + \overline{ABC} (AB + C)$

(iii) What is fan in and fan out ?

*[ Turn Over ]*

- (iv) Why Multiplexer is called 'Universal Logic Module'?
- (v) Write down two advantages of CMOS logic families.
- (vi) How X-OR gate used as an inverter ?
- (vii) Compare between combinational and sequential circuits.
- (viii) What are the different 'types' used in VHDL?

2. Answer any *four* questions : 4×5=20

(i) Define the following terms related to digital ICs.

- (a) Noise margin 1
- (b) Propagation delay 'PLH, 'PHL 2
- (c) Set up time 1
- (d) Hold time. 1

(ii) Implement the function  $F(A, B, C) = \sum m(1, 3, 5, 6)$  using decoder. What are the difference between demultiplexer and decoder. 3+2

- (iii) What do you mean by  $32K \times 16$  memory cell?  
How can you expand the memory capacity from  
( $16 \times 4$ ) to ( $32 \times 4$ ). 1+4
- (iv) What is race around condition ? How it can be  
overcome ? 5
- (v) What is Totem-pole arrangement of a TTL  
NAND gate ? Briefly describe it by proper  
circuit diagram. 2+3
- (vi) Briefly discuss about synthesis tools and Test  
benches of VHDL. 5
3. Answer any *one* question : 1×10=10
- (i) (a) Implement the following function using 4 : 1  
MUX only  $f(A, B, C, D) = \Sigma(0, 2, 3, 5, 8,$   
 $9, 12, 14)$  4
- (b) Define register. 2
- (c) What do you mean by structural modelling?  
4
- (ii) (a) Design a synchronous MOD 10 counter.  
10
-

2019

B.Sc. (Hons)

4th Semester Examination

**ELECTRONICS**

Paper - C8T

**(Operational Amplifiers and Applications)**

Full Marks : 40

Time : 2 Hours

*The figures in the margin indicate full marks.  
Candidates are required to give their answers  
in their own words as far as practicable.*

1. Answer any five questions : 2×5=10
- (i) What is OPAMP ?
  - (ii) Explain the term input offset voltage in connection with an OP-AMP.
  - (iii) Draw the equivalent circuit of an OP-AMP.
  - (iv) What is gain-bandwidth product of an OPAMP ?

[ Turn Over ]


- (v) Why does the voltage gain of OPAMP decrease at high frequencies ?
- (vi) What is CMRR ?
- (vii) What is slew rate of an OP-AMP ?
- (viii) Write down the advantage of SMPS over ordinary power supply.

2. Answer any *four* questions :

4×5=20

- (i) Explain how an OPAMP can be used as an adder and a comparator.  $2\frac{1}{2}+2\frac{1}{2}$
- (ii) State the characteristics of an ideal OP-AMP.   
5
- (iii) Draw a unity gain buffer and determine its input and output resistances.  $2+1\frac{1}{2}+1\frac{1}{2}$
- (iv) Draw the ideal voltage transfer characteristics of an OP-AMP and also explain the same.  $2+3$

 - (v) For an inverting OP-AMP circuit (fig. below) determine input current and output voltage for an input-voltage of 2V. 5



- (vi) Draw the circuit of voltage to current converter using OP-AMP and explain its operation. 2+3

3. Answer any *one* question : 1×10=10

- (i) (a) Explain the working principle of a Schmitt Trigger using an OP-AMP.
- (b) Draw the circuit diagram of an active lowpass 1st order Butterworth filter and describe its principle of operation.

5+(2+3)

- (ii) (a) What is phase locked loop ?

[ Turn Over ]

- (b) Draw the block diagram of a phase locked loop (PLL) and explain its principle of operation.
- (c) Discuss how a PLL circuit can be used as a frequency multiplier. 2+4+4
-