

**2018**

**CBCS**

**3rd Semester**

**ELECTRONICS**

**PAPER—C5P**

**(Honours)**

**(Practical)**

*Full Marks : 20*

*Time : 2 Hours*

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

**Semiconductor Devices Lab.**

1. Study the I-V characteristic of a diode in forward bias condition. Find its ac and dc resistance.
2. Study the I-V characteristic of a BJT in CE mode of operation for different values of base current and find  $r_i$ ,  $r_o$  and  $\beta$ . (Symbols have their usual meaning)

*(Turn Over)*

3. Study the J-V characteristics of a BJT in common base mode of operation and find  $r_i$ ,  $r_o$ ,  $\beta$ . Symbols save their usual meaning.
4. Study the static characteristic of JFET ( $I_D$   $V_S$   $V_{DS}$ ) of a common source JFET. Also study its transfer characteristics curve.
5. Study the I-V characteristic of a SCR.
6. Study the I-V characteristics of the common collection configuration of BJT and find voltage gain  $r_i$ , and  $r_o$ .
7. Design p-n junction (ordinary) circuit and obtain I-V characteristics curve.
8. Design zener diode circuit and obtain I-V characteristics curve.
9. Design CE configuration of BJT and obtain  $r_i$ ,  $r_o$  and  $\beta$ .
10. Study the I-V characteristics of CB configuration and obtain voltage gain  $r_i$  and  $r_o$ .
11. Design UJT circuit and study the I-V characteristics.
12. Design SCR circuit and study its I-V characteristics.

13. Study the I-V characteristics curve of JFET.
14. Design MOSFET circuit and obtain I-V characteristics.

*Distribution of Marks :*

Experiment : 15 marks

Laboratory Note Book : 02 marks

Viva-Voce : 03 Marks