

2017

ELECTRONICS

(Basic Circuit Theory and Network Analysis)

[Honours]

(CBCS)

(Practical)

PAPER – C1P

Full Marks : 20

Time : 2 hours

The figures in the right-hand margin indicate marks

Answer any one question, selecting it by a lucky draw

1. Verify Thevenin's theorem by using a resistive Wheatstone bridge network :

(a) Working formula and schematic circuit diagram. } 3

(b) Circuit implementation. } 2

2. Verify Norton's theorem by using a resistive Wheatstone bridge network :
- (a) Working formula and schematic circuit diagram. 3
 - (b) Circuit implementation. 2
 - (c) Data for load voltage (V_L) and load current (I_L). 4
 - (d) Draw I_L - V_L graph and determine I_N and R_N from the graph. 4
 - (e) Discussion and Accuracy. 2
3. Verify Maximum power transfer theorem by using a resistive Wheatstone bridge network :
- (a) Working formula and schematic circuit diagram. 3
 - (b) Circuit implementation. 2
 - (c) Data for load voltage (V_L) and load current (I_L). 4
 - (d) Verification of Maximum Power Transfer theorem from R_L - P curve. 4
 - (e) Discussion and Accuracy. 2

4. Design a first order low pass *RC* filter of cut-off frequency 3 kHz and study its frequency response.
- (a) Theory. 3
 - (b) Circuit diagram and implementation. 2
 - (c) Record Data for gain vs. frequency. 4
 - (d) Draw the gain vs. frequency curve and verify the cut-off frequency. 4
 - (e) Discussion and accuracy. 2
5. Design a first order high pass *RC* filter of cut-off frequency 1 kHz and study its frequency response.
- (a) Theory. 3
 - (b) Circuit diagram and implementation. 2
 - (c) Record Data for gain vs. frequency. 4
 - (d) Draw the gain vs. frequency curve and verify the cut-off frequency. 4
 - (e) Discussion and accuracy. 2

- (c) Data for load voltage (V_L) and load current (I_L). 4
- (d) Draw I_L - V_L graph and determine V_{TH} and R_{TH} from the graph. 4
- (e) Discussion and Accuracy. 2

6. To draw the resonance curve of series *LCR* circuit and to find the *Q*-factor :
- (a) Theory. 3
 - (b) Circuit diagram and implementation. 2
 - (c) Record data for resonance curve (two values of *R*). 4
 - (d) Draw *I-f* curve and calculate *Q* value. 4
 - (e) Discussion and accuracy. 2
7. To study the resonance curve of series *LCR* circuit and to find the *Q*-factor from the ratio of $\frac{V_e}{V_i}$ at resonance :
- (a) Theory. 3
 - (b) Circuit diagram and implementation. 2
 - (c) Record data for resonance curve (two values of *C*). 4
 - (d) Draw *I-f* curve and calculate *Q* value. 3

- (e) Compare Q value from resonance curve and $\frac{V_e}{V_i}$ at resonance. 1
- (f) Discussion and accuracy. 2

Distribution of Marks

Experiment	: 15 marks
Laboratory Note Book	: 02 marks
Viva-voce	: 03 marks
<hr/>	
Total	: 20 marks