

2018

2nd Semester

PHYSICS

(Honours)

PAPER—C3P

(Practical)

Full Marks : 20

Time : 2 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Answer one questions.

1. Determine the capacitance of a given capacitor using an ac source of low frequency (~ 50 Hz)
 - (a) Theory 3
 - (b) Circuit diagram and its implementation 2
 - (c) Table for V_R , V_C data for fixed R and a fixed frequency (at least five voltages). 5

(Turn Over)

- (d) Drawing of $V_C \sim I$ curve. 3
- (e) Determination of capacitance from graph. 1
- (f) Accuracy 1
2. Determine an unknown low resistance using potentiometer.
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Table for null points for at least three different wires. 2×3
- (d) Calculation of r 2
- (e) Accuracy 1
- (f) Discussion 1
3. Determine unknown low resistance using Carey Foster's Bridge.
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Table for determining resistance per unit length (ρ) for at least four sets. 4
- (d) Table for determining unknown resistance (R) for at least four sets. 4
- (e) Calculation 1
- (f) Accuracy 1

4. Verify the Thvenin and Norton theorems
- (a) Statement of the theorems 2
 - (b) Circuit diagram and its implementation 2
 - (c) $V_L \sim I_L$ (load voltage and load current) data for at least six loads. 6
 - (d) Draw two separate graphs for two theorems 2+2
 - (e) Verification summary table 1
5. Verify the Superposition theorem
- (a) Theory 3
 - (b) Circuit diagram and its implementation 2
 - (c) Data for voltage (v) and current (I) when one source is switched on alternatively and both sources are switched on (Two times each) 2×3
 - (d) Calculation 2
 - (e) Verification table and accuracy 2
6. Verify Maximum power transfer theorem
- (a) Theory 3
 - (b) Circuit diagram and its implementation 2
 - (c) Data for $V_L \sim I_L$ or $V_L \sim R_L$ at least for 10 different loads. 5
 - (d) Draw of $P_L \sim R_L$ graph 3

- (e) Conclusion and accuracy 2
7. Determine the resistance of a given galvanometer following Thomson's method.
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Table for the value of the P, Q and R resistance variation and null point detection. 8
- (d) Calculation and accuracy 2
8. Study the variation of magnetic field strength (B) along the axis of a solenoid.
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Measure B along the axis of the given solenoid for a fixed current (at least 10 positions) 5
- (d) Plot variation of B along the axis 3
- (e) Determine $\frac{dB}{dx}$ at two ending points and two mid points. 2
9. Determine self-inductance of a coil by Anderson's bridge (DC balance to be made by the examiner)
- (a) Theory 3

- (b) Circuit diagram and its implementation 2
- (c) Data for variation of ' r ' with at least five different capacitors. 5
- (d) Drawing graph $\frac{1}{c} \sim r$
- (e) Calculation of ' L ' from graph. 3
10. Study the response curve of a series LCR circuit.
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Data for current Vs. frequency graph (at least 10 frequencies) 5
- (d) Draw graph ($I \sim f$) to show resonance point and band width 2
- (e) Determination of impedance at resonance, quality factor and Band width. 3
11. Study the response curve of a parallel LCR circuit and determine its antiresonance frequency
- (a) Theory 3
- (b) Circuit diagram and its implementation 2
- (c) Data for frequency Vs. impedance graph (at least 10 frequencies) 5

- (d) Drawing of frequency Vs. impedance graph 3
- (e) Determine antiresonance frequency and quality factor. 2

LNB—02, Viva-Voce—03
