

M.Sc 3rd Semester Examination 2010

PHYSICS

PAPER—PH-2104

Full Marks : 40

Time : 2 hours

The figures in the right-hand margin indicate marks

(Applied Electronics -Spl.)

PAPER—PH-2104

GROUP—A

[Marks : 20]

Answer Q.No.1 and any one from the rest

1. Answer any *five* bits : 2×5

(a) How can you construct a band-pass filter from a given low-pass filter and a high-pass filter ?
What is the necessary condition ?

(b) Why the gain of a 2nd order Butterworth high-pass filter must be 1.586 ?

(Turn Over)

- (c) What are the characteristics features of a regulated power supply ?
- (d) Explain the use of a D flip-flop as a phase comparator.
- (e) Draw the circuit diagram of a triangular wave generator and write down the expression for the frequency of oscillation.
- (f) Draw the circuit diagram of a logarithmic amplifier and write down the expression for the output voltage in terms of input voltage and circuit parameters.
- (g) Explain the use of operational amplifiers as analog multiplier.
- (h) How frequency multiplication can be done using phase Locked Loop ?
2. (a) What do you mean by instrumentation amplifier? Draw the circuit diagram of an instrumentation amplifier using 3 op-amps and derive the expression for the output voltage.

- (b) What do you mean by a series voltage regulator? Draw the circuit diagram of a series voltage regulator using op-amp as comparator and a power transistor as a pass element. Derive the expression for the output voltage. 1 + 1 + 2
3. (a) Explain the circuit operation of an inverting Schmitt trigger and find out an expression for the hysteresis voltage. 5
- (b) Draw the circuit diagram of a voltage controlled oscillator and derive the expression for the output frequency. 1 + 4

PAPER — PH-2104

GROUP—B


[Marks : 20]

Answer Q.No.1 and any one from the rest

1. Answer any *five* bits : 2 × 5
- (a) ECL gate is much faster than TTL. Justify.
- (b) Design a 2-input CMOS NOR gate.

(c) Give the basic structure of 4:2 Encoder.

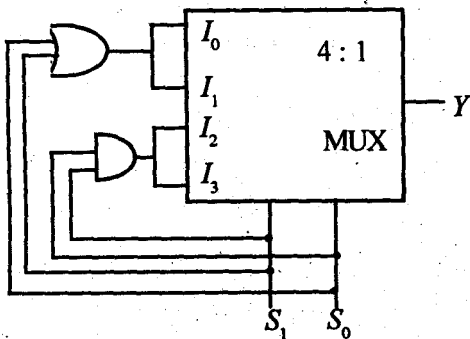(d) Write the different outputs for the following multiplexer circuit.



(e) What do you mean by magneto-optical memory?

(f) What are the advantages of 'totem pole' connection in TTL gate?

(g) What are the special features of EEPROM?

2. (a) Give the basic structure of "two phase ratio-less dynamic shift" register.

(b) 'CCD memory is a sequential memory': Justify this statement.

(c) Show how to design a 1:10 demultiplexure and state how it works.

4 + 3 + 3

3. (a) What do you mean by I^2L gate ?
- (b) Give the example of wire'd logic by proper circuit diagram.
- (c) How the fan out is increased in TTL from DTL gate ?
- (d) How do you convert 'octal number' to binary number ? Give the required block diagram.
- 2 + 2 + 3 + 3

(*Solid State Phy- Spl.*)

PAPER — PH-2104

[*Marks : 40*]

Answer **Q.No.1** and any **three** from the rest

1. Answer any *five* bits : 2 × 5
- (a) Draw the first three bands in a simple cubic lattice in [110] on the basis of empty lattice approximation.
- (b) What is the origin of plasmon in a solid.

- (c) How Fermi surface shape can be determined experimentally in a metal?
- (d) Explain why polarization direction changes in a perovskite structure as the temperature is lowered.
- (e) Explain why lattice defects are inevitable in solids.
- (f) Explain the mechanism of the formation of F -center in a solid.
- (g) Find the shortest burger vector corresponding to stable dislocation in a B.C.C crystal.
2. (a) Derive Thomas Fermi dielectric function assuming an electron gas to an electrostatic field.
- (b) Explain what is meant by soft optical phonon.
- (c) Show the variation of W vs. K for a polariton.
- $$7 + 1\frac{1}{2} + 1\frac{1}{2}$$
3. (a) Derive energy of electron in a solid according to TBA. (Tight Binding Approximation)

- (b) Find the bandwidth in a b.c.c crystal in 110 direction according to TBA. 8 + 2
4. (a) Derive the dispersion relation for a tightly bound exciton.
- (b) Describe in details the mechanism of Thermo-luminescence in a solid. 5 + 5
5. (a) Find an expression of conductivity in an ionic crystal.
- (b) What is screw dislocation ? Find an expression of dislocation energy in this case. 5 + 5
6. (a) Find an expression of dipolar polarizability assuming a dielectric in an alternating field.
- (b) Show that the transition in Rochelle salt follows first order characteristics. 4 + 6