

M.Sc. 2nd Semester Examination, 2015

PHYSICS

PAPER— PHS-204(A & B)

Full Marks : 40

Time : 2 hours

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

PHS-204(A)

[Marks : 20]

Answer **Q. No. 1** and any **one** from the rest

1. Attempt any *five* of the following : 2 × 5
- (a) Draw the circuit diagram of an AC light dimmer using Triac and Diac.
 - (b) Explain the advantages of a phototransistor over photodiode as a light sensor.

(Turn Over)

- (c) Draw the circuit diagram of a constant- k band-stop filter and state the condition for which it will act as a constant- k band-stop filter.
- (d) Define iterative impedance of a network and find out its expression for a T -network.
- (e) A network is connected with a source having the internal impedance $R + j\omega R_1$, and a load Z_L in series. For which Z_L the load will be driven by the maximum power from the source. Justify your answer.
- (f) When can you call two networks equivalent?
- (g) When can you call a transmission line loss-less and why?
- (h) What is quantum efficiency of a photo-diode?
2. (a) Design a shunt type foster network equivalent to a circuit having a pole at $\omega_1 = 1$ megaradians/sec and a zero at $\omega_2 = 1.5$

megaradians/sec. The input impedance of the circuit is $j 1000$ ohms at 0.8 megaradians/sec. 5

(b) Explain how a given Π network can be converted into its equivalent T form with necessary derivations. 5

3. (a) Derive telegrapher's equations and solve it to derive the general expression for voltage and current at any point along the length of a transmission line. 6

(b) Derive the condition for developing a distortion less line. 4

PHS-204(B)

[Marks : 20]

Answer Q. No. 1 and any one from the rest

1. Answer any five questions : 2 x 5

(a) Show that MUX is an universal gate.

(b) What are the differences between RAM/ROM and storage memory ?

- (c) What will be the content of the accumulator of 8085 microprocessor after the execution of following instructions :

	<u>Hex Code</u>
MVI B	06
HALT	76
MOV A, B	78

- (d) What is aliasing effect in sampling process ?
How it can be overcome ?
- (e) What is tri state Buffer ?
- (f) Represent the following Boolean function using a 8 : 1 MUX
 $F(0, 3, 5, 8, 9, 11, 12, 14)$
- (g) What are the advantages of digital communication over analog communication ?
- (h) What is S/H circuit ? How sampling is done using the circuit ?

2. (a) Explain steps and timing of data flow using timing diagram when instruction code (MOV C, A - 4 F_H) stored in a location 2005_H, is fetched in case of 8085 microprocessor.
- (b) How data bus and address bus are demultiplexed? 6 + 4
3. (a) With the help of circuit diagram explain how analog voltage is converted to digital voltage in a dual slope A/D converter.
- (b) What is quantisation process and the associated error?
- (c) Define resolution and settling time in connection with D/A converter. 5 + 3 + 2