

2022

1st Semester Examination

**ELECTRONICS**

Paper : ELC 104

(Analog Electronics)

Full Marks : 40

Time : Two Hours

*The figures in the margin indicate full marks.  
Candidates are required to give their answers  
in their own words as far as practicable.*

Answer any *four* questions each from Group-A and Group-B; and *two* question from Group-C.



**Group - A**

Answer any *four* questions. 2×4=8

1. Write two advantages of MOSFET. 2
2. Draw the circuit diagram to build a NAND gate using diode. 2
3. Write virtual ground concept in case of OP-AMP. 2

P.T.O.

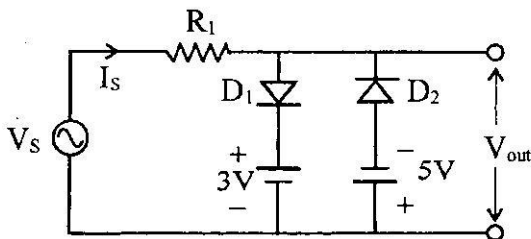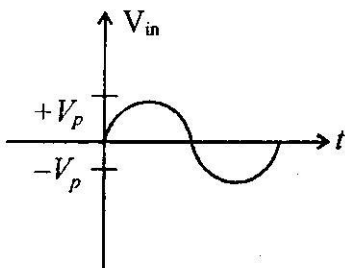4. Draw the output waveform for the circuit and input waveform are given below : 2




5. What is thermal runaway? 2
6. Draw the small signal model of a n-channel enhancement type MOSFET without channel length modulation effect. 2

### Group - B

Answer any *four* questions. 4×4=16

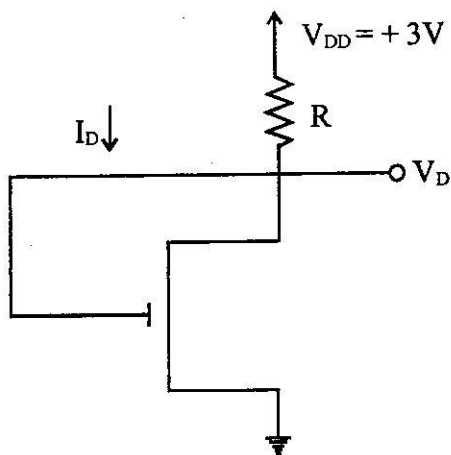7. Consider the circuit given below and find the value of  $R$  to obtain a current  $I_D$  of  $80\mu\text{A}$ . Also find the dc voltage  $V_0$ . Assume the NMOS transistor threshold voltage  $V_t = 0.6\text{V}$  and  $\mu_n c_{ox} = 200\mu\text{A}/\text{V}^2$ .  $L = 0.8\mu\text{m}$ ,  $W = 4\mu\text{m}$ , neglect the channel length modulation effect (i.e assume  $\lambda = 0$ ). 4



8. Draw voltage transfer curve of a MOSFET. Indicate and explain different operation regions of the MOSFET. 1+3
9. Draw and explain emitter follower circuit. 2+2
10. Explain log amplifier using proper circuit diagram. 2+2
11. Draw different topologies of a feedback amplifier. 4
12. Implement  $Y = \overline{(AB + CD + E)}$  using CMOS logic. 4

### Group - C

Answer any *two* questions : 8×2=16

13. Define Q point and its stabilization in a dc output characteristics. What are the different types of stabilization method? Explain voltage divider bias method using proper circuit diagram. 1+1+2+1+3

P.T.O.

14. Write ideal characteristics of Op-amp. Draw and explain instrumentation amplifier. 2+2+4
15. Draw and explain triangular wave generator circuit using Op-amp. Gives input-output waveforms. (2+4)+2
16. Draw and explain source follower amplifier using small signal model of a MOSFET. Find out the expression of input resistance, output resistance and gain. (2+3)+3
-