

M.Sc. 1st Semester Examination, 2023

ELECTRONICS

(Analog Electronics)

PAPER — ELC-104

Full Marks : 50

Time : 2 hours

Answer **all** questions

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

GROUP—A

Answer any **four** questions : 4×2

1. Draw an AND gate using diode only. 2
2. Draw small signal Π model of a MOSFET. 2

3. Write two advantages of SMPS over linear regulated power supply. 2
4. Define common-mode rejection ratio (CMRR) of an op-amp. 2
5. Draw an inverter circuit using PMOS and N-MOS. 2
6. What are the necessary condition of an oscillator circuit? 2

GROUP – B

Answer any **four** questions : 4 × 4

7. Draw a biased clipper circuit. Give input output waveforms. 2 + 2
8. Draw four feedback topologies used in electronic circuits. 1 + 1 + 1 + 1


9. Draw and explain series regulator circuit using op-amp. 2 + 2
10. How MOSFET acts as an amplifier and switch? Show it by using voltage transfer curve. 2 + 2
11. Explain the operation of a phase-shift oscillator with the help of a circuit diagram. 3 + 1
12. Describe the use of an op-amp as an integrator. 4

GROUP – C


Answer any **two** questions : 2 × 8

13. Define stabilization. What are the techniques of stabilization? Figure below shows a silicon transistor with $\beta = 100$ and biased by base resistor method. Determine the operating point. 2 + 3 + 3

(4)

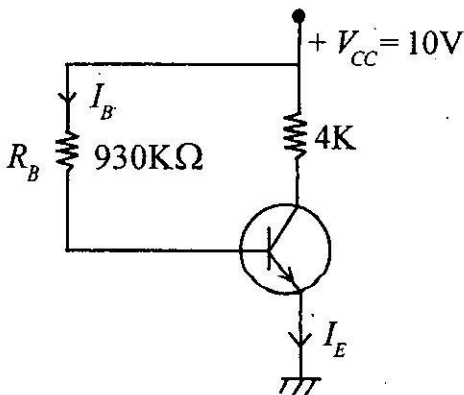

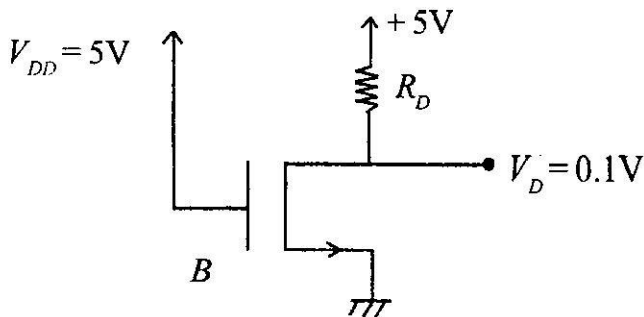14. (a) A circuit is given below. What is the effective resistance between drain and source at the operating point. $V_t = 1\text{V}$, $K_n'(W/L) = 1\text{mA/V}^2$.



(b) Draw $I_D - V_{DS}$ characteristics curve of a n -channel enhancement type MOSFET. Show the different operating regions.

4 + (1 + 3)

15. What is the Schmitt trigger circuit? Draw schematically an op-amp Schmitt trigger and explain its operation.

2 + 2 + 4

16. What is Darlington connection? Compare between an emitter follower and a Darlington pair. Discuss the high frequency effects in a transistor.

2 + 2 + 4

[Internal Assessment – 10 Marks]
