

M.Sc. 2nd Semester Examination, 2023

ELECTRONICS

(Digital Electronics Lab)

[Practical]

PAPER – ELC-295

Full Marks : 50

Time : 3 hours

Candidates are required to give their answers in their own words as far as practicable

Answer any one question selecting it by a Lucky draw

- 1. Design and implement a full adder circuit using NAND gates only.**
- 2. Design and implement a full subtractor circuit using NAND gates only.**

(Turn Over)

3. Design and implement a full adder circuit using 4 : 1 Mux.
4. Design and implement a full subtractor circuit using 4 : 1 Mux.
5. Design and implement a binary to Gray code converter circuit.
6. Design and implement a J-K and M-S flip flops.
7. Design and implement a MOD-8 counter.
8. Design and implement a MOD-10 counter.
9. Design and implement a BCD adder.

Marks Distribution

Circuit design	: 15 Marks
Implementation	: 10 Marks
Results & Discussion	: 10 Marks
Viva-voce	: 10 Marks
LNB	: 05 Marks
<hr/>	
Total	: 50 Marks