

**PG 1st Semester Examination, 2023****PHYSICS**

PAPER — PHS-104.1 &amp; 104.2

*Full Marks : 50**Time : 2 hours**The figures in the right hand margin indicate marks**Candidates are required to give their answers in their own words as far as practicable***PAPER — PHS-104.1***( Analog Electronics )***(Attempt Q1, Q2 and any one from the rest)****GROUP — A**

1. Attempt any *two* of the following questions :  $2 \times 2$
- (a) What is skip distance in radio wave propagation ?

- (b) Define the terms : Tropospheric Waves, Surface wave propagation.
- (c) Define slew rate of an Op-Amp. What is it's value for an ideal Op-Amp ?
- (d) Why TV and FM radio waves cannot propagate through long distances ?

GROUP – B

1. Attempt any *two* of the following questions : 4 × 2
- (a) Explain the method of generation of Single Side Band (SSB) signal using phase cancellation method. Draw the waveform of SSB signal.
  - (b) With necessary block diagram, explain the operation of a superheterodyne FM radio receiver. Write the value of intermediate frequency used in FM receiver.
  - (c) Draw the circuit diagram of emitter coupled differential amplifier and derive the condition for which it will offer infinite CMRR.

- (d) Explain the operation of Doppler RADAR.
3. (a) Draw the circuit diagram of a current mirror circuit using low  $\beta$  transistors and show that it will behave as a current mirror circuit deriving the necessary mathematical expression. 4
- (b) Derive RADAR range equation. 4
4. (a) Explain the operation of Foster Seeley discriminator for the demodulation of FM signals with the drawing of the necessary circuit diagram. 5
- (b) Explain the method of generation of stereo FM signal. Also show how we can recover the L and R audio signals at the stereo FM receivers. 3

**PAPER – PHS-104.2**


*( Digital Electronics-I )*

## GROUP – A

1. Answer any *two* bits :

2 × 2

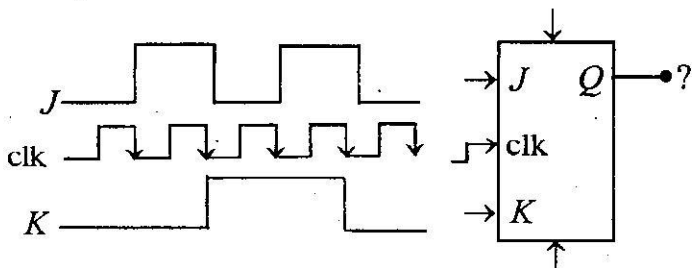(a) Draw the waveform of the following output



- (b) What will be maximum frequency of the clock pulse that can be used in a 4-bit asynchronous counter? consider the  $t_{pd}$  for each flipflop is 10 nano second.
- (c) Draw the Karnangh map for a 4 bit circuit which receives BCD input and gives high output when input is in odd number.
- (d) Draw a circuit which can convert a 5kHz signal into 1kHz signal.


## GROUP – B

2. Answer any *two* bits : 4 × 2

(a) Draw the circuit of a synchronous 3-bit up/down counter and explain the operation briefly.

(b) (i) What do you mean by SIPO register ?

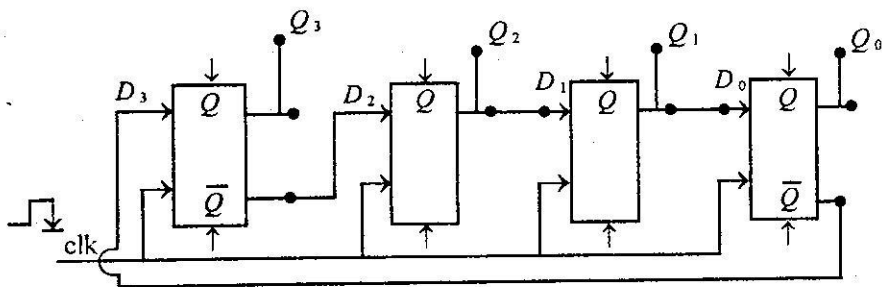(ii) Explain the output states of the following circuit. Assume initially 1 + 3  
 $Q_3 = Q_2 = Q_1 = Q_0 = 0$



(c) (i) What do you mean by as table multivibrator ?

(ii) Draw a circuit, using 555 timer IC, to produce a square wave of frequency 15 KHz.

(d) Convert a D flipflop into T flipflop.

### GROUP - C


3. Answer any *one* bits :

8 × 1

(a) (i) Write down the excitation table of T flipflop.

(ii) Using T flip-flops design a synchronous counter circuit which has the following output states

2 + 6

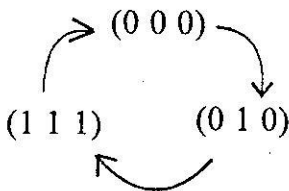


(b) (i) Solve the following digital equation by Karnanagh map

$$Y = \prod_m (0, 3, 4, 7, 8).d(11, 12, 15)$$

( 7 )

(ii) Draw a circuit to check two signals  $A(A_1 A_0)$  and  $B(B_1 B_0)$  are equal or not.

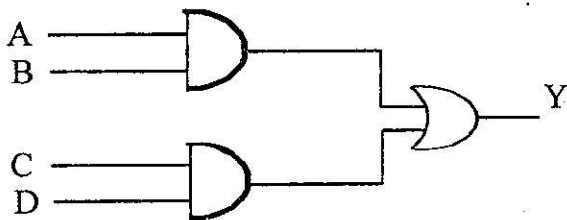(iii) Design the following circuit with NAND gates. 3 + 3 + 2



[ Internal Assessment – 10 Marks ]

---