

M.Sc. 2nd Semester Examination, 2025

ELECTRONICS

(Digital System Design)

PAPER – ELC-203

Full Marks : 50

Time : 2 hours

Answer any **four** questions each from Group-A and Group-B and **two** questions from Group-C.

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

GROUP – A


Answer any **four** questions : 2×4

1. Implement NAND gate using diode and transistor only. Write its truth table. $1 + 1$

(Turn Over)

(2)

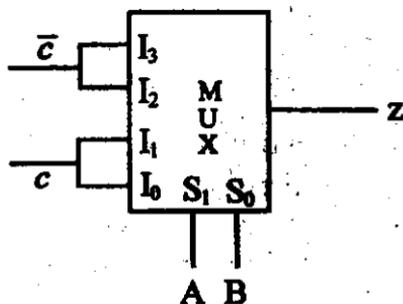2. Implement XOR gate using NOR gates only.
3. Write advantages of ECL logic families.
4. The MUX shown below is a 4×1 MUX, what is the output of the MUX ?



5. Implement $y = \overline{A(B+C)}$ using CMOS logic.
6. Write two differences between combinational circuit and sequential circuit. 1 + 1

GROUP - B

Answer any four questions : 4 × 4

7. Convert JK flip flop to T flip flop.
8. Simplify the following Boolean expression using k map.

$$f = \sum m(0,1,2,3,5,7,8,9,10,12,13)$$

9. Write different types of shift registers with suitable diagram. 1 + 1 + 1 + 1

10. Design 2-bit magnitude comparator circuit. Explain its operation with truth table. 1 + (2 + 1)

11. Implement $f = \sum m(0,3,5,8,9,10)$ using 4:1 MUX.

12. Design 4-bit binary to Gray code converter circuit.

GROUP – C

Answer any two questions : 8 × 2

13. Differentiate between asynchronous and synchronous counter. Design MOD 6 synchronous counter. Write two applications of a counter. 2 + 4 + 2

14. What is race around condition ? How it can be avoided ? Write different states of a ring counter using suitable circuit diagram. 2 + 3 + 2 + 1

15. (i) An 8-bit D/A converter has output voltage range of 0V to 255V. Find the resolution of the system.

(ii) Differentiate between weighted resistor D/A converter and R-2R ladder type D/A converter.

(iii) Write the operation of successive approximation type A/D converter using suitable block diagram. 2 + 2 + 4

(5)

16. Explain Mealy and Moore machines with suitable examples. 4 + 4

[Internal Assessment — 10 Marks]

